



Australia's  
Global  
University



## ELEC 2141 Digital Circuit Design

Assignment 1 has one design problem with the following the marking breakdown.

### 1. Design approach: (20 marks)

- Clearly explain the design approach (are you using functional blocks? hierarchical design? Five or four variable k-maps?) (8)
- Any assumptions made must be explicitly stated (2)
- You may concisely re-write the specification including your design assumptions if needed (10)

### 2. Formulation: (20 marks)

- Draw any truth table required and clearly indicate input and output columns (10)
  - If appropriate "Do not care conditions" are not used, two marks will be deducted
  - Wrong Truth table – deduct 5 marks
- Show any hierarchical block diagram if used.
- If Boolean function is generated directly from the specification, explain how you arrive at the Boolean function and clearly indicate the function. (10)
  - Boolean function – 5 marks
  - Correct explanation – 5 marks

### 3. Optimization: (20 marks)

- Show all K-maps used and indicate clearly which essential prime implicants or prime implicants are selected in your optimized Boolean expression (16)
  - If the Boolean expression is not correct or not optimized correctly, 1 mark will be deducted per expression
- If multi-level circuit implementation is employed, show the optimization steps
- Indicate GIC of your optimized design (4)

### 4. Circuit implementation (20 marks)

- Draw logic diagram. It should be neat and clearly labelled (inputs and outputs) (14)
- Clearly indicate your choice of implementation (NAND only, NOR only etc) (6)

### 5. Verification (20 marks)

- Draw the schematics of your implementation in Xilinx ISE
- Provide the Verilog test file – (10)
- Include the simulation result from Xilinx (attach the file or screenshots in pdf format). It has to clearly show the waveforms for all inputs and output. – (10)